

- Anshu Arun Ghate
- Cassie Chong Kenci
- Christy Lau Jin Yun (50.002 POC)
- Li Si Hui Brenda
- Tan Lay Lin
- Win Tun Kyaw


50.002 - Optimising an Adder

Part 1

Structure

Our goal is to optimise a 32 bit adder with delay being under 3ns.

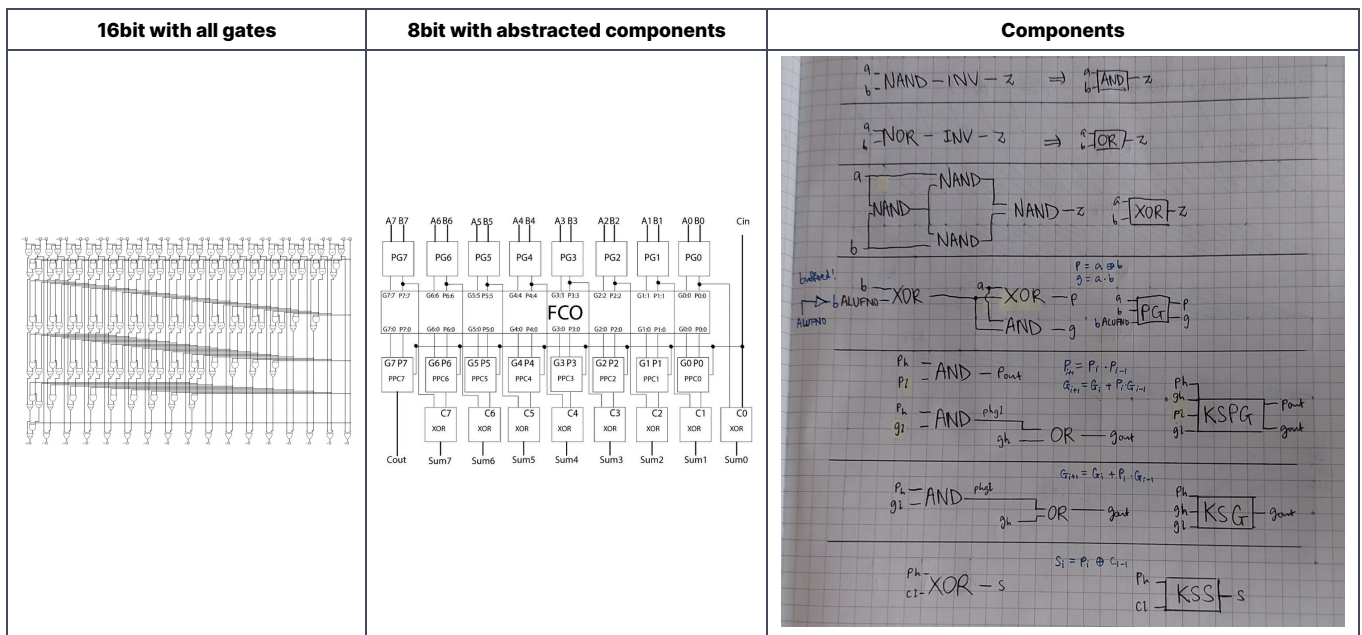Inspired by Kogge-Stone adder, our adder architecture comprises of gates arranged in a tree-like structure to allow parallel computation of addition, be using propagated and generated signals to calculate carry instead of relying on the previous output bit's carry out as done in a ripple carry adder.



32 bit adder consists of 1 **PG** layer, 5 **KSPG** and **KSG** layers, one last layer for one **KSG** for the carry out, and one **sum** layer to compute the sum bits. Lastly, **g**, **h** and **n** are computed from the results of the adder.

What was done

All **AND**, **XOR** and **OR** gates were remade with inverting logic.

The most loaded signal **ALUFN0** is buffered.

[Kogge-Stone architecture](#) was chosen to allow for parallel prefix adding to speed up computation as compared to ripple carry adders.

Stats

Fastest timing of adder: 2.814ns

Circuit size: 1337 gates

Minimum observed setup = 829.52ps

Part 2

We chose the 8th bit for easier computation.

A BC file is created from the circuit design, which is then converted into a CNF file by using the telegram submission bot.

The CNF file is fed into **findsolssat.jar** and UNSAT result is true.

```
C:\Users\chris\Downloads>java -jar findsolssat.jar Compareadders.cnf
Unsat : true

C:\Users\chris\Downloads>_
```